



中山大學  
SUN YAT-SEN UNIVERSITY



# 计算机组成原理

## 第三章：计算机中的运算

中山大学计算机学院  
陈刚

2022年秋季

# 本讲内容

## □ 基本运算


- 加法和减法

- 位操作


## □ 乘法运算

## □ 除法运算

## □ 浮点运算

 

# Review: 2's Complement

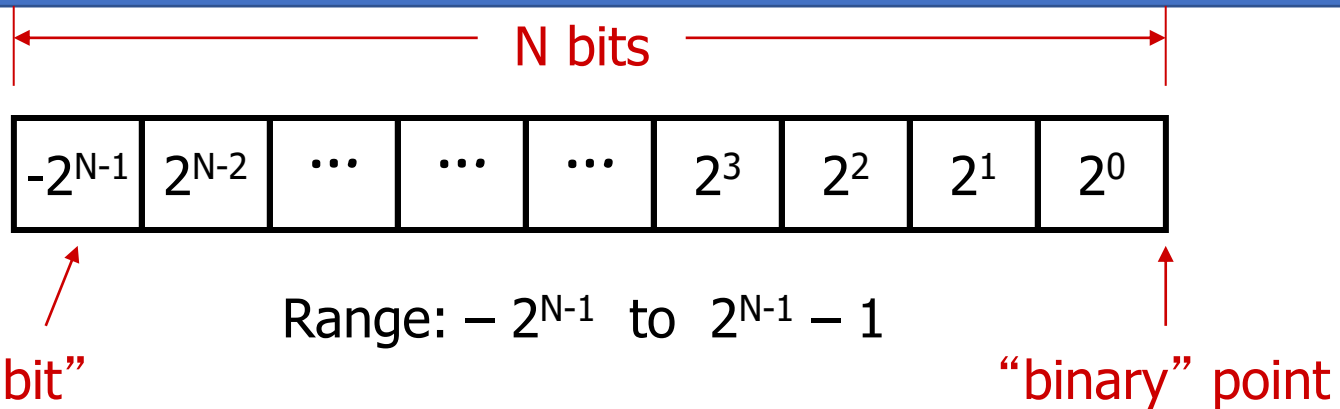

□ 8-bit 2's complement example:

$$11010110 = -128 + 64 + 16 + 4 + 2 = -42$$

□ Beauty of 2's complement representation:

□ same binary addition procedure will work for adding both signed and unsigned numbers

□ as long as the leftmost carry out is properly handled/ignored

□ Insert a "binary" point to represent fractions too:

$$1101.0110 = -8 + 4 + 1 + 0.25 + 0.125 = -$$

# Binary Addition

## Example of binary addition “by hand” :

Adding two N-bit numbers produces an (N+1)-bit result

A: 1101  
B: + 0101  
-----  
10010



Carries from previous column

## Let's design a circuit to do it!

Start by building a block that adds one column:

called a “full adder” (FA)

 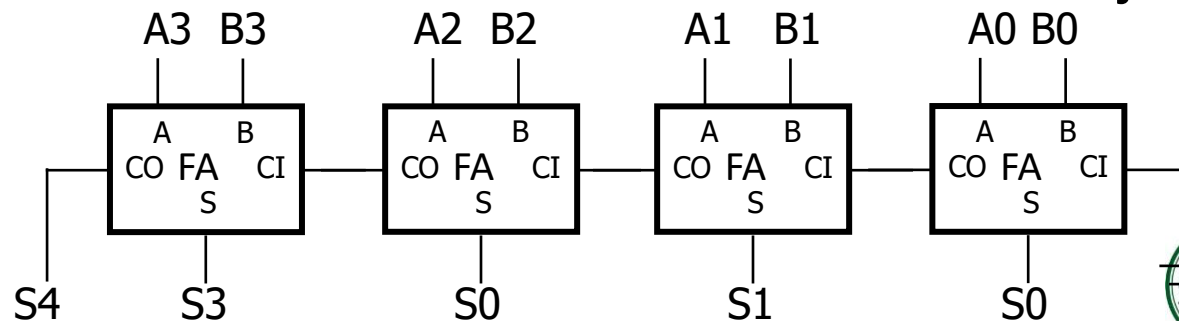Then cascade them to add two numbers of any size...



# Designing an Adder (1位全加器)

真值表:

$C_i$	$A$	$B$	$C_o$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

□ Follow the step-by-step method

1. Start with a truth table:
2. Write down eqns for the “1” outputs:


$$C_o = \overline{C_i}AB + C_i\overline{A}B + C_iA\overline{B} + C_iAB$$

$$S = \overline{C_i}\overline{A}B + \overline{C_i}A\overline{B} + C_i\overline{A}\overline{B} + C_iAB$$

3. Simplifying a bit (seems hard, but experienced designers are good at this art!)

$$C_o = C_i \cdot (A \oplus B) + A \cdot B$$

$$S = C_i \oplus (A \oplus B)$$

 

# For Those Who Prefer Logic Diagrams


▣ A little tricky, but only 5 gates/bit!

$$C_o = C_i \cdot (A \oplus B) + A \cdot B$$

$$S = C_i \oplus (A \oplus B)$$

XOR的真值表:

X	Y	X <u>XOR</u> Y
0	0	0
0	1	1
1	0	1
1	1	0

 

# Subtraction: $A - B = A + (-B)$

□ Subtract B from A = add 2's complement of B to A

□ In 2's complement:  $-B = \sim B + 1$  ←  $\sim$  = bit-wise complement




□ Let's build an arithmetic unit that does *both* add and sub

□ operation selected by *control input*:

1表示减, 0表示加, 1与1异或为0, 0与1异或为1, 相当于取反

Subtract  
1表示减, 作为进位输入, 相当于加1

 

# Condition Codes

- One often wants 4 other bits of information from an arith unit:
  - Z (zero): result is = 0
    - big NOR gate
  - N (negative): result is < 0
    - $S_{N-1}$
  - C (carry): indicates that most significant position produced a carry, e.g., “1 + (-1)”
    - Carry from last FA
  - V (overflow): indicates answer doesn't fit

precisely: 
$$V = A_{i-1}B_{i-1}\bar{N} + \bar{A}_{i-1}\bar{B}_{i-1}N$$

-or-

$$V = CO_{i-1} \oplus CI_{i-1}$$

To compare A and B, perform A-B and use condition codes:

Signed comparison:

LT  $N \oplus V$

LE  $Z + (N \oplus V)$

EQ Z

NE  $\sim Z$

GE  $\sim (N \oplus V)$

GT  $\sim (Z + (N \oplus V))$


Unsigned comparison:

LTU C

LEU  $C + Z$

GEU  $\sim C$

GTU  $\sim (C + Z)$

 



# Carry and Overflow Examples

- We can have carry without overflow and vice-versa
- Four cases are possible (Examples are 8-bit numbers)

$$\begin{array}{r}
 \phantom{+} \phantom{0000} 1 \\
 \begin{array}{|c|c|c|c|c|c|c|c|} \hline 0 & 0 & 0 & 0 & 1 & 1 & 1 & 1 \\ \hline \end{array} \quad 15 \\
 + \begin{array}{|c|c|c|c|c|c|c|c|} \hline 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ \hline \end{array} \quad 8 \\
 \hline
 \begin{array}{|c|c|c|c|c|c|c|c|} \hline 0 & 0 & 0 & 1 & 0 & 1 & 1 & 1 \\ \hline \end{array} \quad 23 \\
 \text{Carry} = 0 \quad \text{Overflow} = 0
 \end{array}$$

$$\begin{array}{r}
 \phantom{+} 1 \phantom{0000} 1 \phantom{0000} 1 \phantom{0000} 1 \phantom{0000} 1 \\
 \begin{array}{|c|c|c|c|c|c|c|c|} \hline 0 & 0 & 0 & 0 & 1 & 1 & 1 & 1 \\ \hline \end{array} \quad 15 \\
 + \begin{array}{|c|c|c|c|c|c|c|c|} \hline 1 & 1 & 1 & 1 & 1 & 0 & 0 & 0 \\ \hline \end{array} \quad 248 \text{ (-8)} \\
 \hline
 \begin{array}{|c|c|c|c|c|c|c|c|} \hline 0 & 0 & 0 & 0 & 0 & 1 & 1 & 1 \\ \hline \end{array} \quad 7 \\
 \text{Carry} = 1 \quad \text{Overflow} = 0
 \end{array}$$



$$\begin{array}{r}
 \phantom{+} \phantom{0000} 1 \\
 \begin{array}{|c|c|c|c|c|c|c|c|} \hline 0 & 1 & 0 & 0 & 1 & 1 & 1 & 1 \\ \hline \end{array} \quad 79 \\
 + \begin{array}{|c|c|c|c|c|c|c|c|} \hline 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ \hline \end{array} \quad 64 \\
 \hline
 \begin{array}{|c|c|c|c|c|c|c|c|} \hline 1 & 0 & 0 & 0 & 1 & 1 & 1 & 1 \\ \hline \end{array} \quad 143 \text{ (-113)} \\
 \text{Carry} = 0 \quad \text{Overflow} = 1
 \end{array}$$

$$\begin{array}{r}
 \phantom{+} 1 \phantom{0000} 1 \phantom{0000} 1 \\
 \begin{array}{|c|c|c|c|c|c|c|c|} \hline 1 & 1 & 0 & 1 & 1 & 0 & 1 & 0 \\ \hline \end{array} \quad 218 \text{ (-38)} \\
 + \begin{array}{|c|c|c|c|c|c|c|c|} \hline 1 & 0 & 0 & 1 & 1 & 1 & 0 & 1 \\ \hline \end{array} \quad 157 \text{ (-99)} \\
 \hline
 \begin{array}{|c|c|c|c|c|c|c|c|} \hline 0 & 1 & 1 & 1 & 0 & 1 & 1 & 1 \\ \hline \end{array} \quad 119 \\
 \text{Carry} = 1 \quad \text{Overflow} = 1
 \end{array}$$

# 溢出检测

- 溢出：结果超出了正常的表示范围（太大 和 太小）
  - 例如：- 8 < = 4位二进制数 <= 7
- 当对具有不同符号的操作数进行加法运算时，不会出现溢出！
- 当进行下列加法时，出现溢出：
  - 两个正数相加，结果为负
  - 两个负数相加，结果为正
- 溢出可以用如下方法检测：
  - 输入到最大位的进位 != 从最大位输出的进位


(Carry into MSB != Carry out of MSB )

  

# Overflow Detection Logic

$$\text{Overflow} = \text{CarryIn}[N-1] \text{ XOR } \text{CarryOut}[N-1]$$


溢出检测逻辑

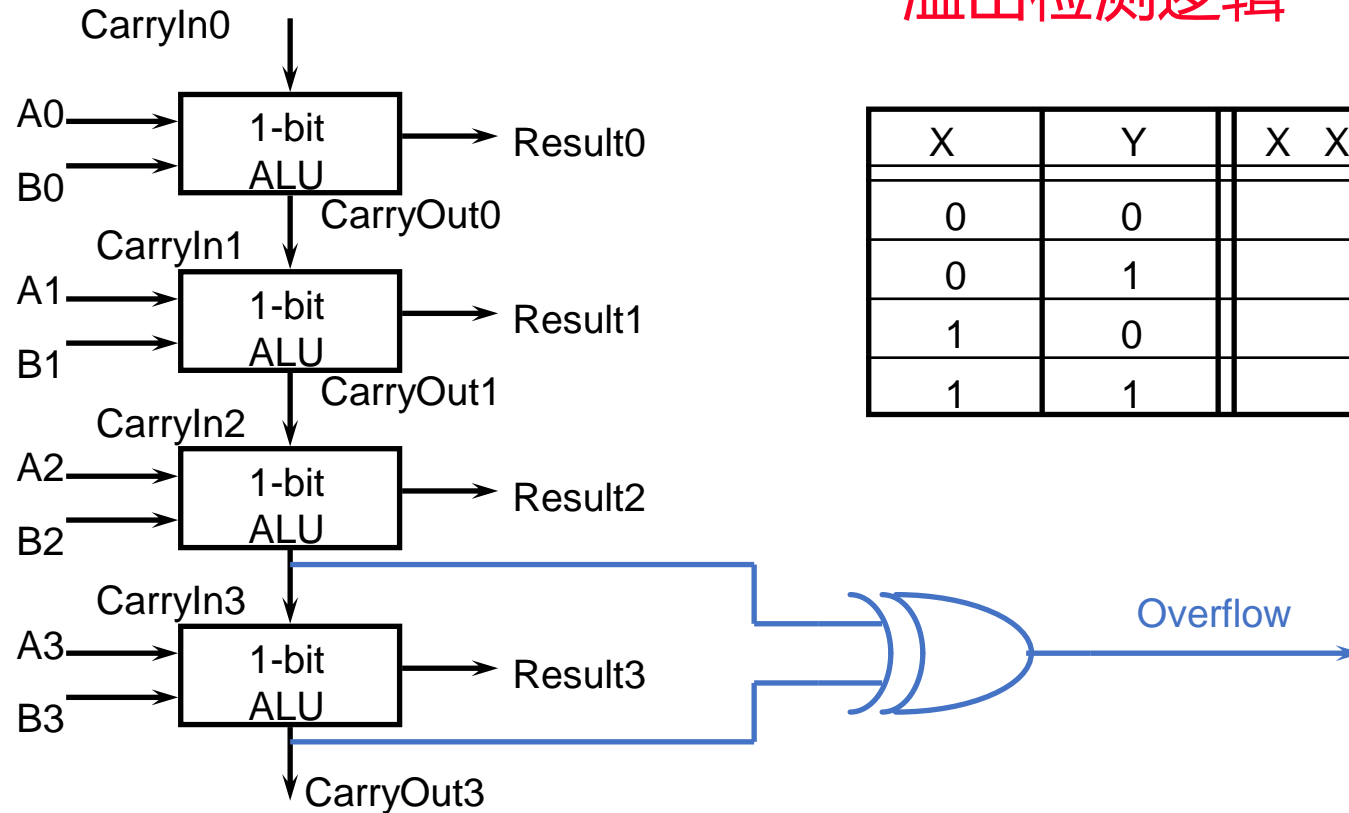

X	Y	X XOR Y
0	0	0
0	1	1
1	0	1
1	1	0
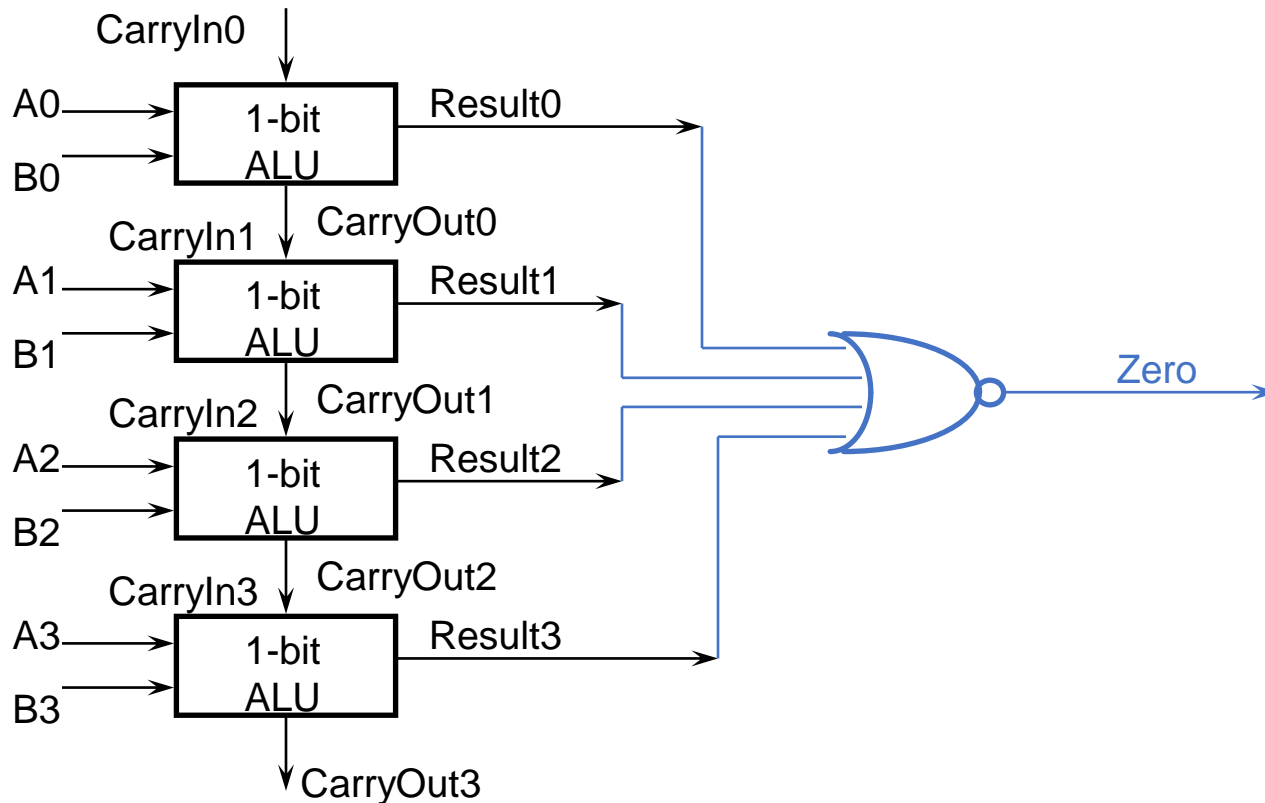
# Zero Detection Logic


- Zero Detection Logic is a one BIG NOR gate (support conditional jump)



```


* `timescale 1ns / 1ps
* //////////////////////////////////////
* module addsub
* #(parameter WIDTH=8)      //指定数据宽度参数, 缺省值是8
* (
*     input [(WIDTH-1):0] a,    // 缺省位数由参数WIDTH决定
*     input [(WIDTH-1):0] b,
*     input sub,                // =1为减法
*     output [(WIDTH-1):0] sum,
*     output cf,                // 进位标志
*     output ovf,               // 溢出标志
*     output sf,                // 符号标志
*     output zf                 // 为0标志
* );
* wire [(WIDTH-1):0] subb,subb1;
*     wire cf2; // 进位
*     assign subb1 = b ^ {WIDTH{sub}}; // 对于减法是取反
*     assign subb = subb1 + sub; // 对于减法是加1, sub=1(减法)sub=0(加法)
*
*     assign {cf2,sum} = a + subb;
*     assign sf = sum[WIDTH-1];
*     assign zf = (sum == 0) ? 1 : 0 ;
*     assign cf = cf2 ^ sub;
*     assign ovf = (a[WIDTH-1] ^ sum[WIDTH-1]) & (subb[WIDTH-1] ^ sum[WIDTH-1]);
*
* endmodule

```

 
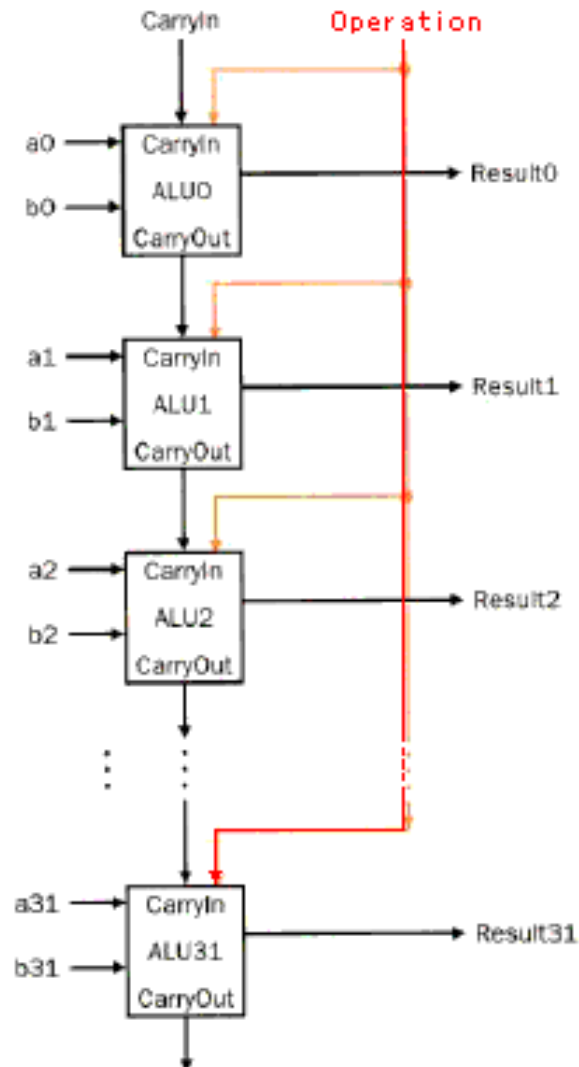
# Basic 32 bit ALU

- Inputs parallel
- Carry is cascaded
- Ripple carry adder
- Slow, but simple
- 1st Carry In = 0



# Set on Less Than

## □ Functions

- AND

- OR

- Add

- Subtract

## □ Missing: comparison


- Slt rd, rs, rt

- If  $rs < rt$ ,  $rd=1$ , else  $rd=0$   $N \oplus V? \quad ? \quad ?$

- All bits = 0 except the least significant

- Subtraction ( $rs - rt$ ), if the result is negative  $\rightarrow$   
 $rs < rt$

- Use of sign bit as indicator N

 

## ❑ Missing: comparison

- ❑ Slt rd, rs, rt

- ❑ If  $rs < rt$ ,  $rd=1$ , else  $rd=0$   $N \oplus V? \quad ? \quad ?$

- ❑ All bits = 0 except the least significant

- ❑ Subtraction ( $rs - rt$ ), if the result is negative  $\rightarrow rs < rt$

- ❑ Use of sign bit as indicator N

- ❑ Why  $N \oplus V? \quad ? \quad ?$  Why requires to check the overflow?


## ❑ Consider:

- ❑ case 1:  $rs < 0$ ,  $rt > 0$ , ( $rs < rt$ )

- ❑ case 2  $rs > 0$ ,  $rt < 0$ , ( $rs > rt$ )

- ❑ If no overflow occurs, case 1: N is 1; case 2: N is 0

 - ❑ If overflow occurs, case 1: N is 0; case 2: N is 1





# Condition Codes

One often wants 4 other bits of information from an arith unit:

□ Z (zero): result is = 0

□ big NOR gate

□ N (negative): result is < 0

□  $S_{N-1}$

□ C (carry): indicates that most significant position produced a carry, e. g., “1 + (-1)”

□ Carry from last FA

□ V (overflow): indicates answer doesn't fit

□ precisely: 
$$V = A_{i-1}B_{i-1}\bar{N} + \bar{A}_{i-1}\bar{B}_{i-1}N$$

-or-

$$V = CO_{i-1} \oplus CI_{i-1}$$

To compare A and B, perform A-B and use condition codes:

Signed comparison:

LT  $N \oplus V$

LE  $Z + (N \oplus V)$

EQ Z

NE  $\sim Z$

GE  $\sim (N \oplus V)$

GT  $\sim (Z + (N \oplus V))$


Unsigned comparison:

LTU C

LEU  $C + Z$


GEU  $\sim C$

GTU  $\sim (C + Z)$

 

# Extended 1 bit ALU


□ ALU bit with input for Less data

 

AND  
OR  
Add Subtract  
less

# Most significant bit

- Set for comparison
- Overflow detect

 

# Complete ALU

## \* Input



- A
- B

## \* Control lines

- Binvert
- Operation
- Carryin

## \* Output

- Result
- Overflow

 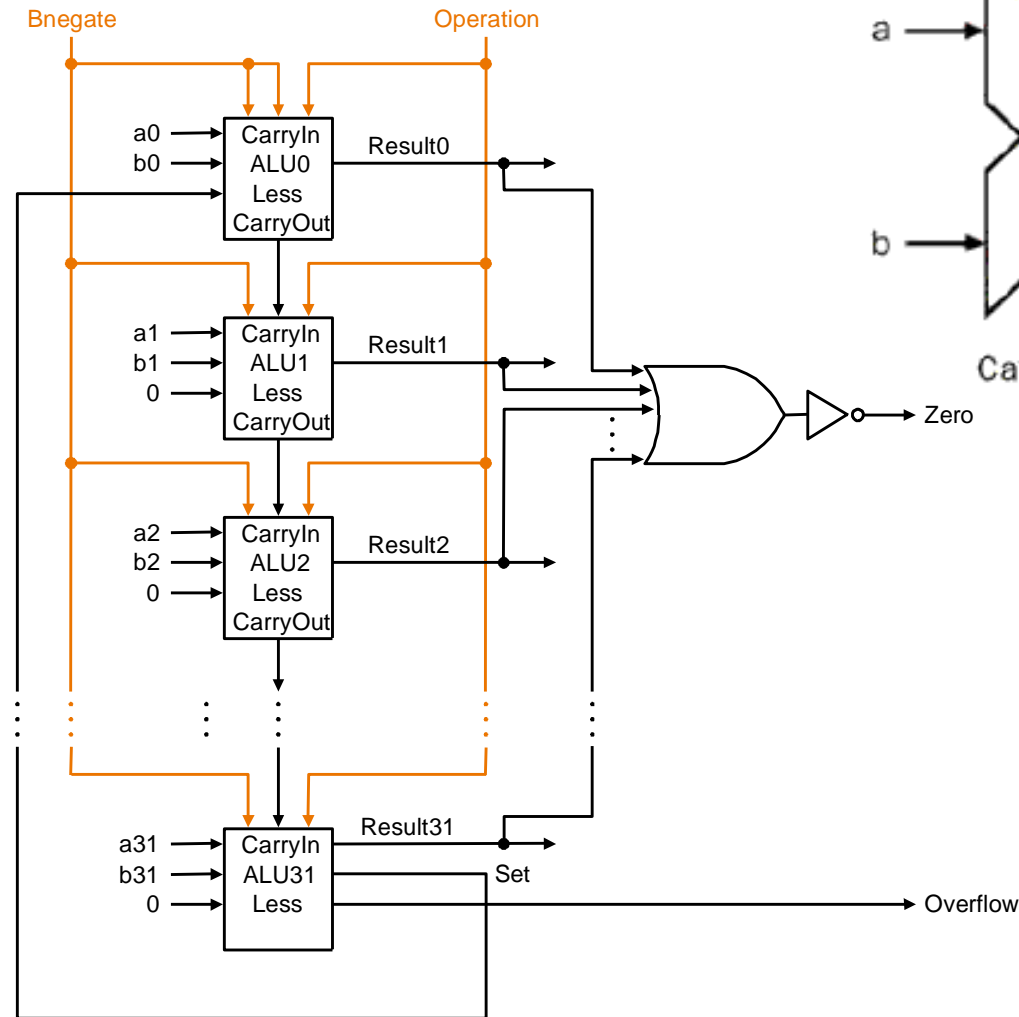


## 行波进位加法器 (Ripple Carry Adder)

- 加位将从最小位(LSB)传播到最大位(MSB)
- N位加法器在最坏情况下的延迟:  $2N$ 个门延迟

$$C_o = C_i \cdot (A \oplus B) + A \cdot B$$

$$S = C_i \oplus (A \oplus B)$$

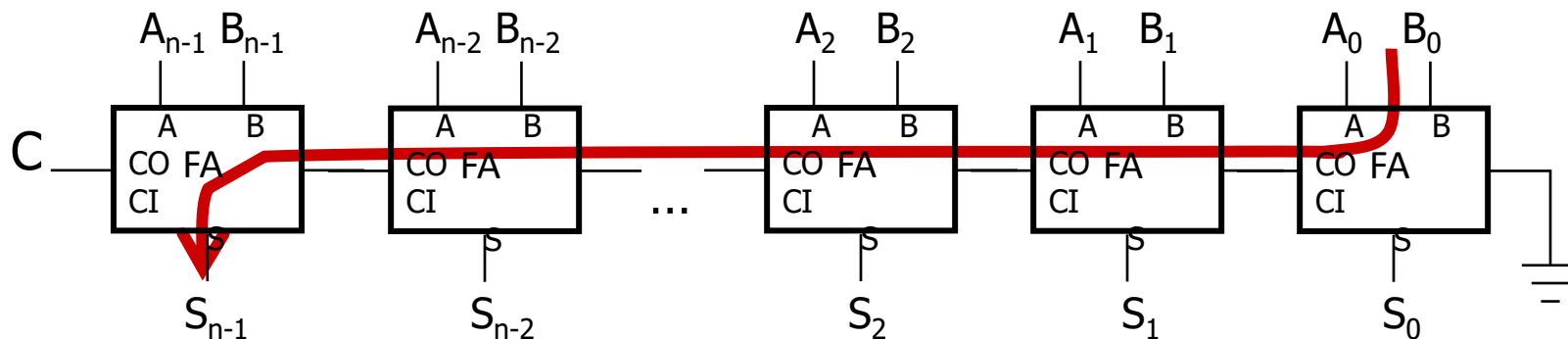

Worse-case path: carry propagation from LSB to MSB, e.g., when adding 11...111 to 00...001.

$$t_{PD} = (t_{PD,XOR} + t_{PD,AND} + t_{PD,OR}) + (N-2) * (t_{PD,OR} + t_{PD,AND}) + t_{PD,XOR}$$



$$\approx \Theta(N)$$

$\Theta(N)$  is read “order N” and tells us that the latency of our adder grows in proportion to the number of bits in the operands.

$$C_o = C_i \cdot (A \oplus B) + A \cdot B$$

$$S = C_i \oplus (A \oplus B)$$

$t(n)$

  

$$\Rightarrow t(12) = \cancel{t_{AND}} t_{XOR} + t_{AND} + t_{OR}$$

$$t(n) = t(n-1) + t_{OR} + t_{AND}$$


$$\Rightarrow t(n) = (t_{OR} + t_{AND}) \cdot (n-1) + t(12)$$

$$= \cancel{t_{OR}} t_{XOR} + t_{AND} + t_{OR} + (n-1)(t_{OR} + t_{AND})$$

$$\Rightarrow t_{PD} = t(n) + t_{OR} = \cancel{t_{OR}}$$

# 但是，性能如何呢？

➤ n位行波进位加法器的关键路径为CP

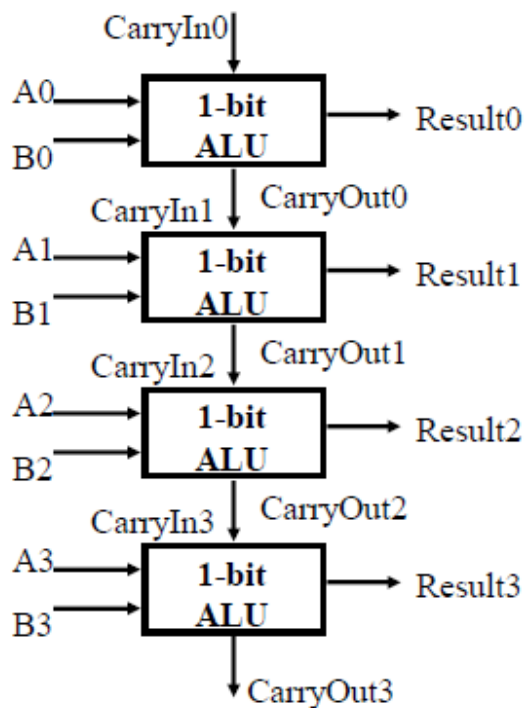

Carry Propagation

设计技巧: 减少关键路径上的硬件延迟

# Fast adders

## 并行加法器 - - 并行进位 (或先行进位)

□ All functions can be represented in 2-level logic.

□ But:

□ The number of inputs of the gates would drastically rise

□ Target:

Optimum between speed and size

$$C_o = C_i \cdot (A \oplus B) + A \cdot B$$

$$S = C_i \oplus (A \oplus B)$$

令: Generate Carry at Bit i:

$$g_i = A_i \cdot B_i$$

Propagate Carry via Bit i:

$$p_i = A_i \text{ xor } B_i$$


## 并行进位的特点

同时产生进位  
加法延时缩短  
实现相对复杂

$$C_{in1} = g_0 + (p_0 \cdot C_{in0})$$

$$C_{in2} = g_1 + (p_1 \cdot g_0) + (p_1 \cdot p_0 \cdot C_{in0})$$
 
$$C_{in3} = g_2 + (p_2 \cdot g_1) + (p_2 \cdot p_1 \cdot g_0) + (p_2 \cdot p_1 \cdot p_0 \cdot C_{in0})$$





# 先行进位 (Carry Lookahead) 的理论基础续

$$C_o = C_i \cdot (A \oplus B) + A \cdot B$$

$$S = C_i \oplus (A \oplus B)$$

✱ Now define two new terms:

- Generate Carry at Bit i:  $g_i = A_i \cdot B_i$
- Propagate Carry via Bit i:  $p_i = A_i \oplus B_i$

第i位产生的进位  $g_i = A_i \& B_i$


通过第i位的传播进位(Propagate Carry)  $p_i = A_i \oplus B_i$

✱ We can rewrite:

- $C_{in1} = g_0 + (p_0 \cdot C_{in0})$
- $C_{in2} = g_1 + (p_1 \cdot g_0) + (p_1 \cdot p_0 \cdot C_{in0})$
- $C_{in3} = g_2 + (p_2 \cdot g_1) + (p_2 \cdot p_1 \cdot g_0) + (p_2 \cdot p_1 \cdot p_0 \cdot C_{in0})$

✱ Carry going into bit 3 is 1 if

 - 进入第3位的进位是1, 如果在第2位, 产生了进位( $g_2$ )
- 或者在第1位产生了进位( $g_1$ )并且 第2位传播了这个进位( $p_2 \& g_1$ )
- 或者在第0位产生了进位( $g_0$ )并且 第1位和第2位都传播了这个进位( $p_2 \& p_1 \& g_0$ )
- 或者在第0位有输入进位( $C_{in0}$ ) 并且 第0位、第1位和第2位都传播了这个进位( $p_2 \& p_1 \& p_0 \& C_{in0}$ )



# Four bit carry look ahead adder

$$\square c1 = g0 + (p0 * c0)$$

$$\square c2 = g1 + p1 * c1 = g1 + (p1 * g0) + (p1 * p0 * c0)$$

$$\square c3 = g2 + p2 * c2 = g2 + (p2 * g1) + (p2 * p1 * g0) + (p2 * p1 * p0 * c0)$$

$$\square c4 = g3 + p3 * c3 = g3 + (p3 * g2) + (p3 * p2 * g1) + (p3 * p2 * p1 * g0) + (p3 * p2 * p1 * p0 * c0)$$


COMMENT:

This kind of adder will be faster than the ripple carry adder, and smaller than the adder with the tow-level logic.


**PROBLEM:**

**If the number of the adder bits is very large, this kind of adder will be too large. So we must seek more efficient ways.**

设置P和G两个先行进位输出端

 


## 并行进位链

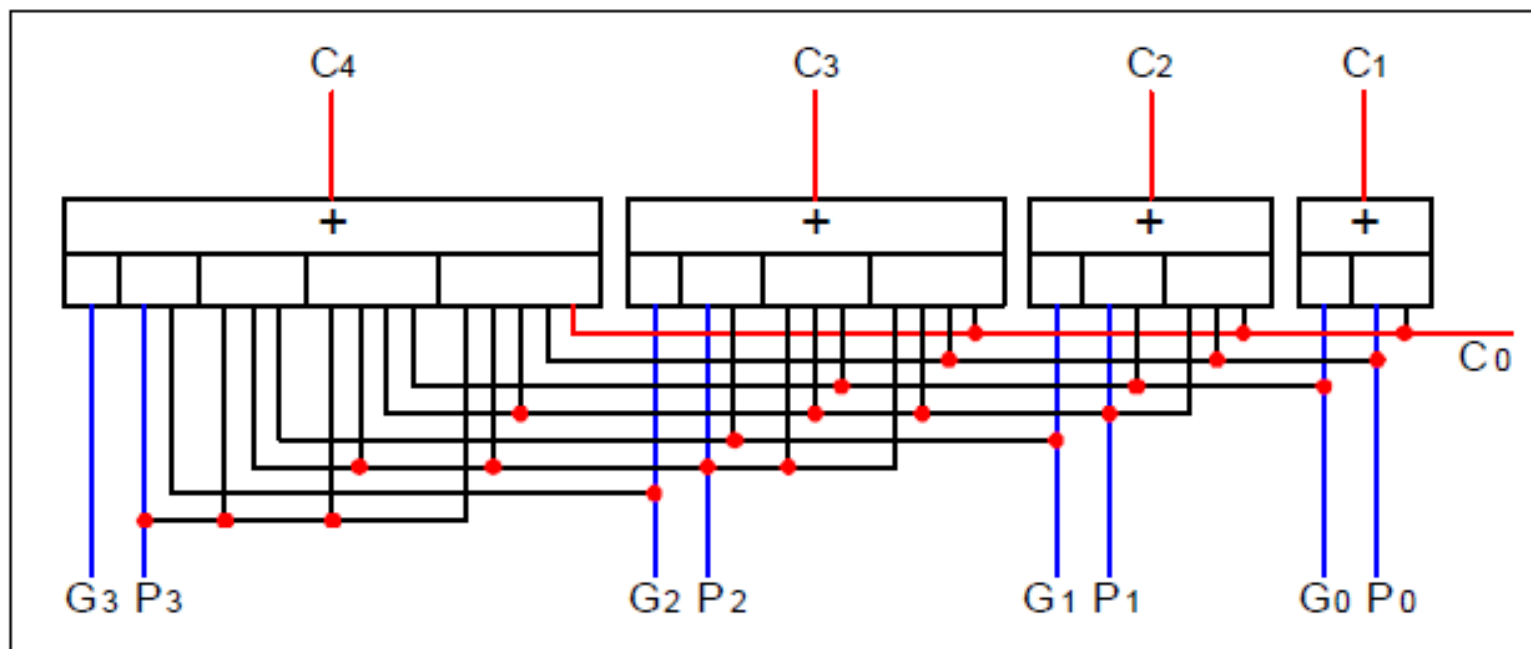


设置P和G两个先行进位输出端

# 并行进位加法器

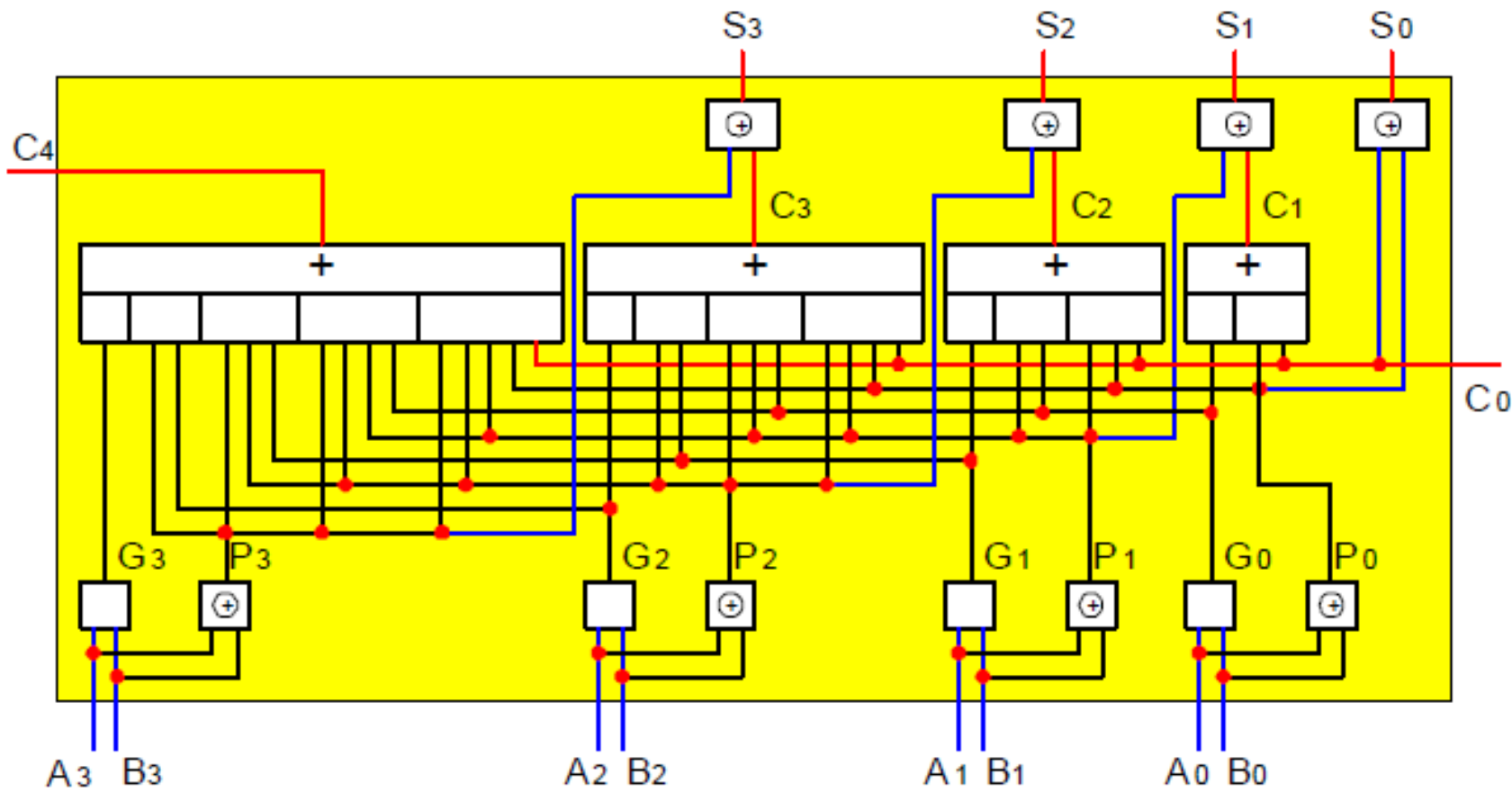


$$C_o = C_i \cdot (A \oplus B) + A \cdot B$$

$$S = C_i \oplus (A \oplus B)$$

 
 
# 局部(级联)先行进位加法器 (Partial Carry Lookahead Adder or Cascaded Carry Lookahead)

- 实现全先行进位加法器的成本太高
  - 想象Cin31的逻辑方程的长度
- 一般性经验:
  - 连接一些N位先行进位加法器, 形成一个大加法器
  - 例如: 连接4个8位进位先行加法器, 形成1个32位局部先行进位加法器




分组并行进位加法器(组内并行, 组间传递)

# Hybrid CLA + Ripple carry

分组并行进位加法器（组内并行，组间并行）



Realisation: Ripple carry adders and

Carry look ahead logic

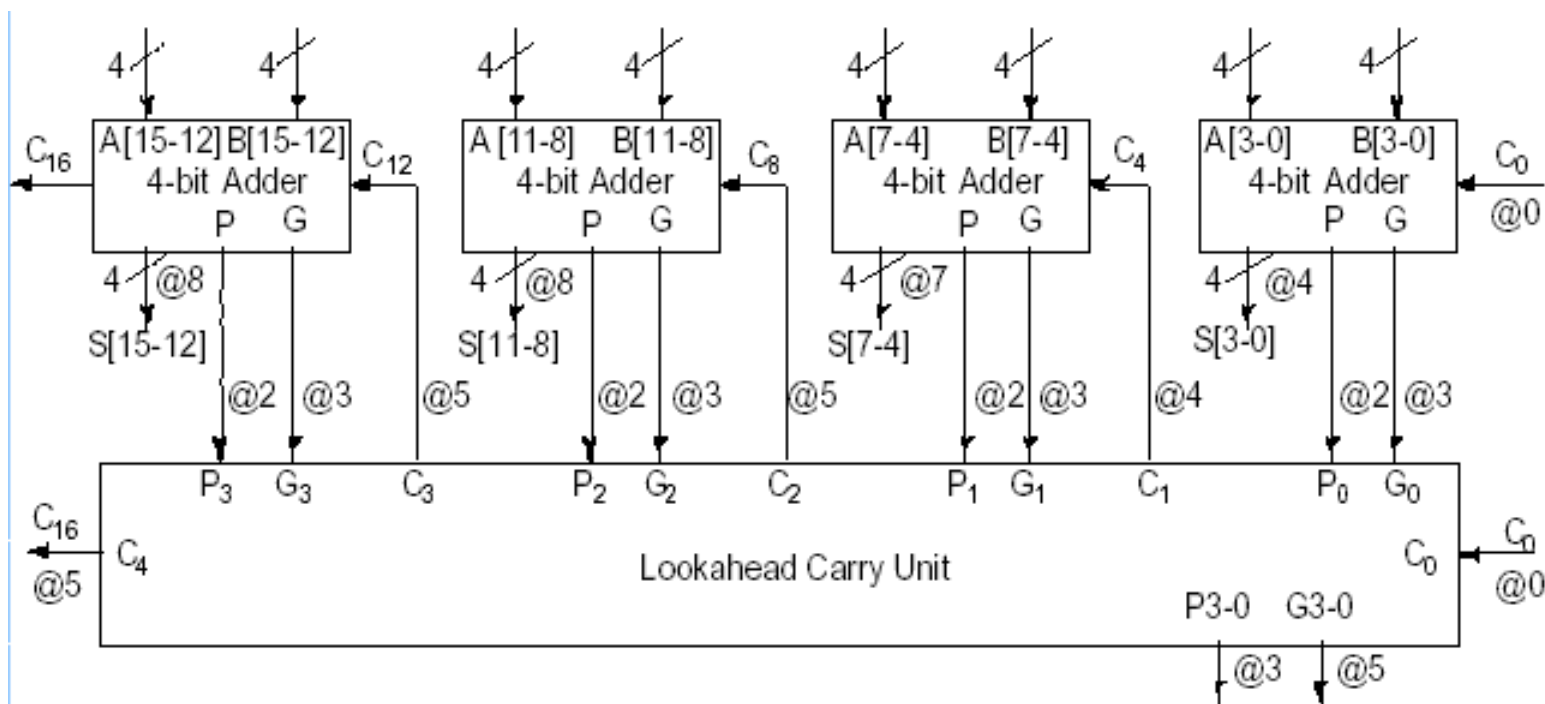
 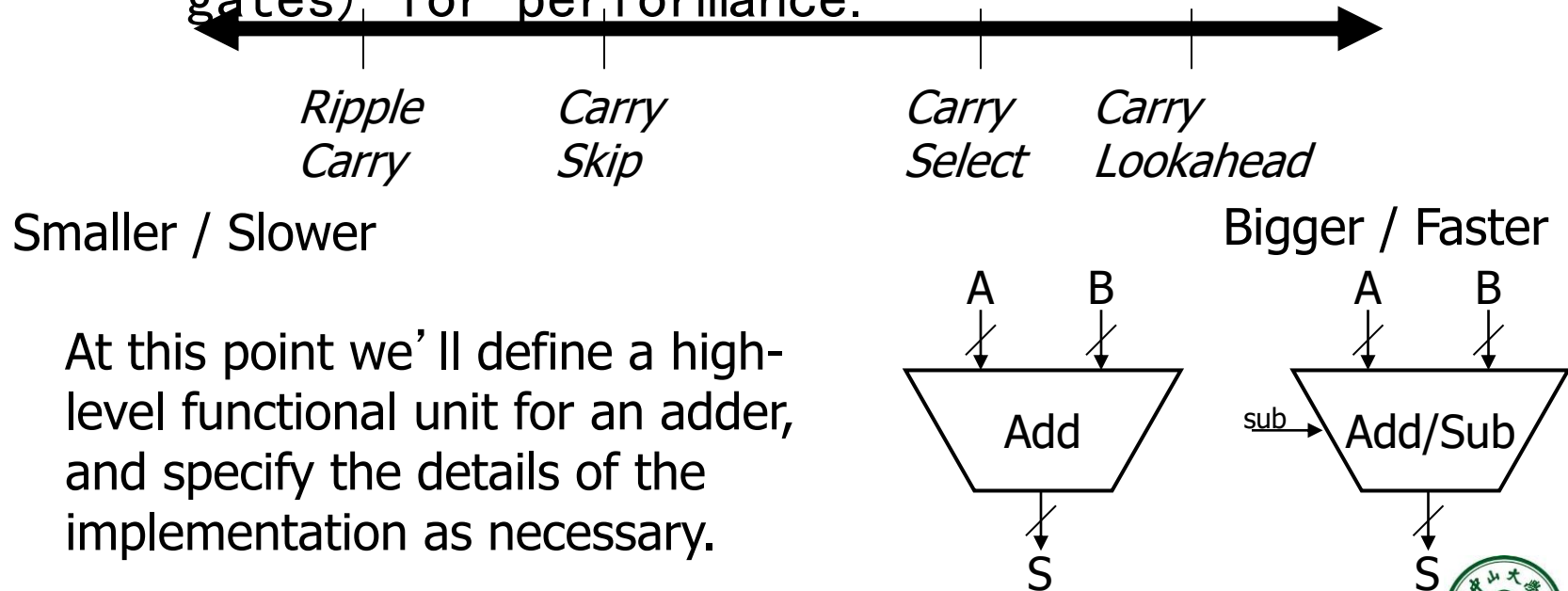
# Adder Summary

- Adding is not only common, but it is also tends to be one of the most time-critical of operations
- As a result, a wide range of adder architectures have been developed that allow a designer to tradeoff complexity (in terms of the number of gates) for performance.



# Shifting Logic

- Shifting is a common operation

- applied to groups of bits

- used for alignment

- used for “short cut” arithmetic operations

- $X \ll 1$  is often the same as  $2 * X$

- $X \gg 1$  can be the same as  $X / 2$

- For example:

- $X = 20_{10} = 00010100_2$

- Left Shift:



- $(X \ll 1) = 0010100\textcolor{red}{0}_2 = 40_{10}$

- Right Shift:

- $(X \gg 1) = \textcolor{red}{0}0001010_2 = 10_{10}$

- Signed or “Arithmetic” Right Shift:

  - $(-X \ggg 1) = (11101100_2 \ggg 1) = \textcolor{red}{1}1110110_2 = -10_{10}$





# 三种移位器

逻辑(*logical*) — 移入的数值总是 "0"




算术(*arithmetic*) — 在右移时, 进行符号扩展



循环(*rotating*) — 移出的位又从另一端移入 (在MIPS中不支持)




注: 需要一位移动。特定指令可能要求进行0⇒32位移动!

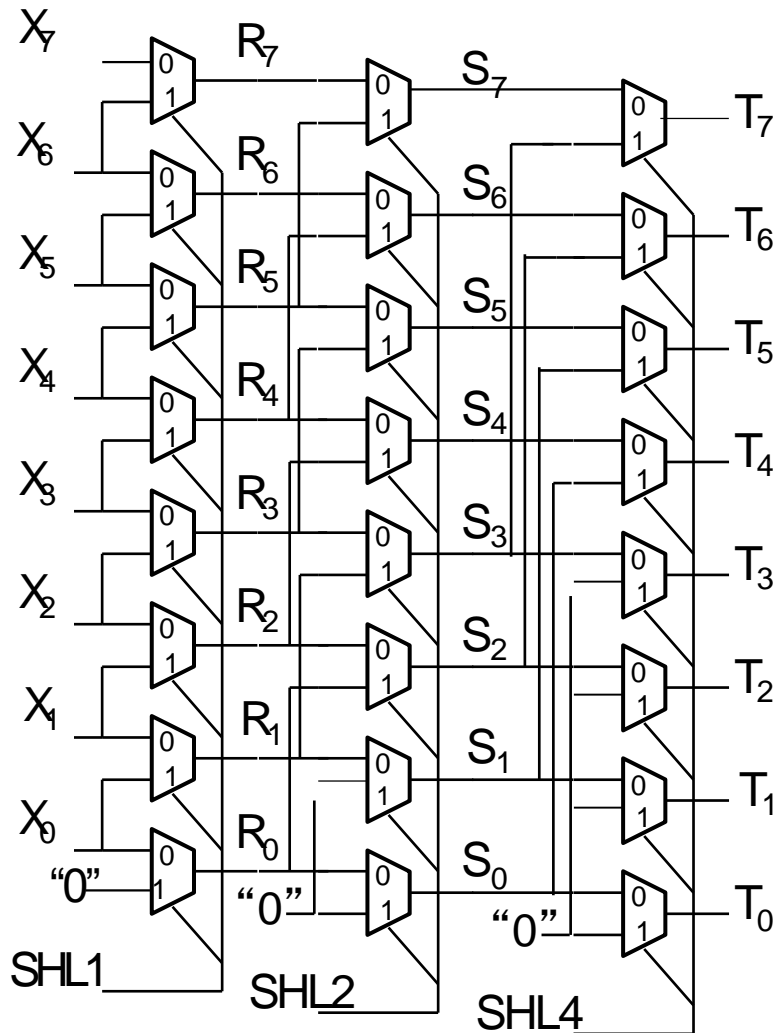

If we connect our “shift-left-two” shifter to the output of our “shift-left-one” we can shift by 0, 1, 2, or 3 bits.


And, if we add one more “shift-left-4” shifter we can do any shift up to 7 bits!

 So, let's put a box around it and call it a new functional block.




# Boolean Operations

- It will also be useful to perform logical operations on groups of bits. Which ones?
  - ANDing is useful for “masking” off groups of bits.
    - ex.  $10101110 \& 00001111 = 00001110$  (mask selects last 4 bits)
  - ANDing is also useful for “clearing” groups of bits.
    - ex.  $10101110 \& 00001111 = 00001110$  (0's clear first 4 bits)
  - ORing is useful for “setting” groups of bits.
    - ex.  $10101110 | 00001111 = 10101111$  (1's set last 4 bits)
  - XORing is useful for “complementing” groups of bits.
    - ex.  $10101110 \wedge 00001111 = 10100001$  (1's invert last 4 bits)
  - NORing is useful for.. uhm...
    - ex.  $10101110 \# 00001111 = 01010000$  (0's invert, 1's clear)

 

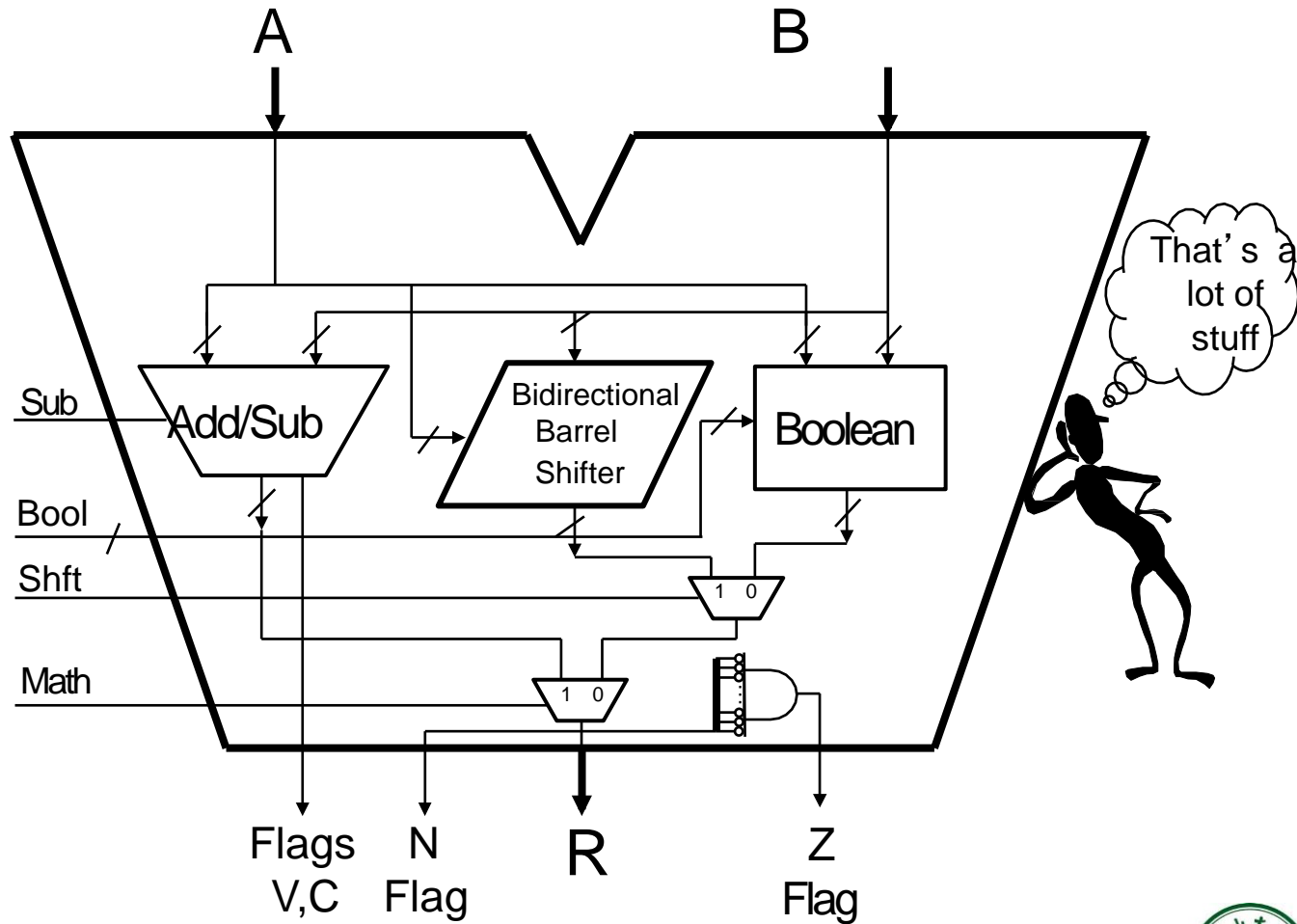
# An ALU, at Last

We give the “Math Center” of a computer a special name-- the Arithmetic Logic Unit.  
For us, it just a big box!


 
# Summary

- ❑ We will use a subset of MIPS instruction set in this class
  - ❑ Sometimes called “miniMIPS”
  - ❑ All instructions are 32-bit
  - ❑ 3 basic instruction formats
    - ❑ R-type – Mostly 2 source and 1 destination register
    - ❑ I-type – 1-source, a small (16-bit) constant, and a destination register
    - ❑ J-type – A large (26-bit) constant used for jumps
  - ❑ Load/Store architecture
  - ❑ 31 general purpose registers, one hardwired to 0, and, by convention, several are used for specific purposes.
- ❑ ISA design requires tradeoffs, usually based on
  - ❑ History, Art, Engineering
  - ❑ Benchmark results



# 联系方式

## □ Acknowledgements:

## □ This slides contains materials from following lectures:

- Computer Architecture (ETH, NUDT, USTC)

## □ Research Area:

- 计算机视觉与机器人应用计算加速,
- 人工智能和深度学习芯片及智能计算机

## □ Contact:

- 中山大学计算机学院
- 管理学院D101 (图书馆右侧)
- 机器人与智能计算实验室
- [cheng83@mail.sysu.edu.cn](mailto:cheng83@mail.sysu.edu.cn)

