

Hardware Description Languages and Verilog

陈刚

副教授

人工智能与无人系统研究所

计算机学院

中山大学



中山大學


SUN YAT-SEN UNIVERSITY

数据科学与计算机学院

School of Data and Computer Science

Constructing State Machines in Verilog

Combinational + Memory = Sequential

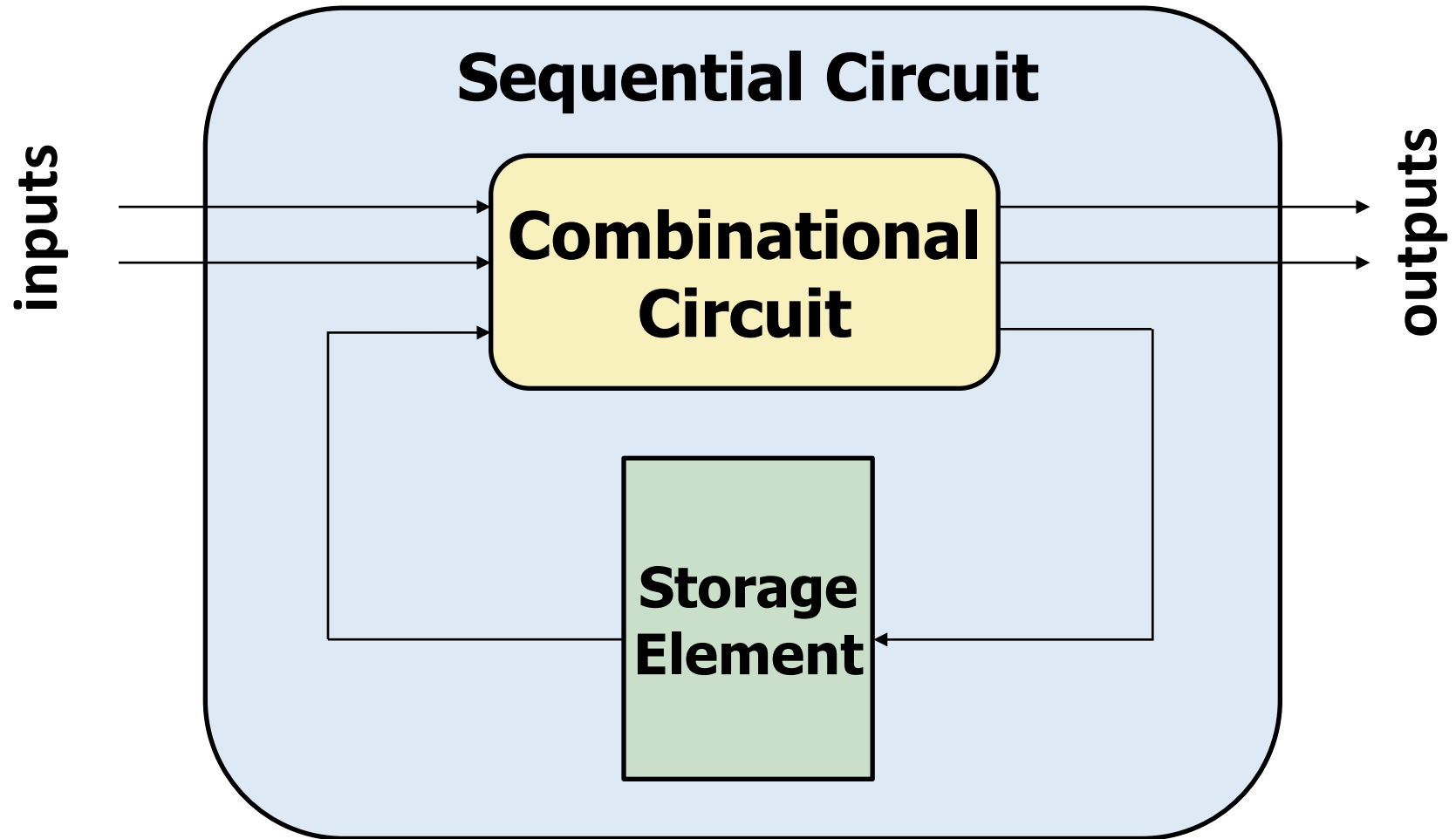

Sequential Logic Circuits

- We have examined designs of circuit elements that can **store information**
- Now, we will use these elements to build circuits that **remember** past inputs



Combinational

Only depends on current inputs



Sequential

Opens depending on past inputs


State

- In order for this lock to work, it has to keep track (**remember**) of the past events!
- If passcode is **R13-L22-R3**, sequence of **states** to unlock:
 - A. The lock is not open (locked), and no relevant operations have been performed
 - B. Locked but user has completed R13
 - C. Locked but user has completed R13-L22
 - D. Unlocked: user has completed R13-L22-R3
- The **state** of a system is a snapshot of all relevant elements of the system at the moment of the snapshot
 - To open the lock, **states A-D must be completed in order**
 - If anything else happens (e.g., L5), lock **returns** to state A



State Diagram of Our Sequential Lock

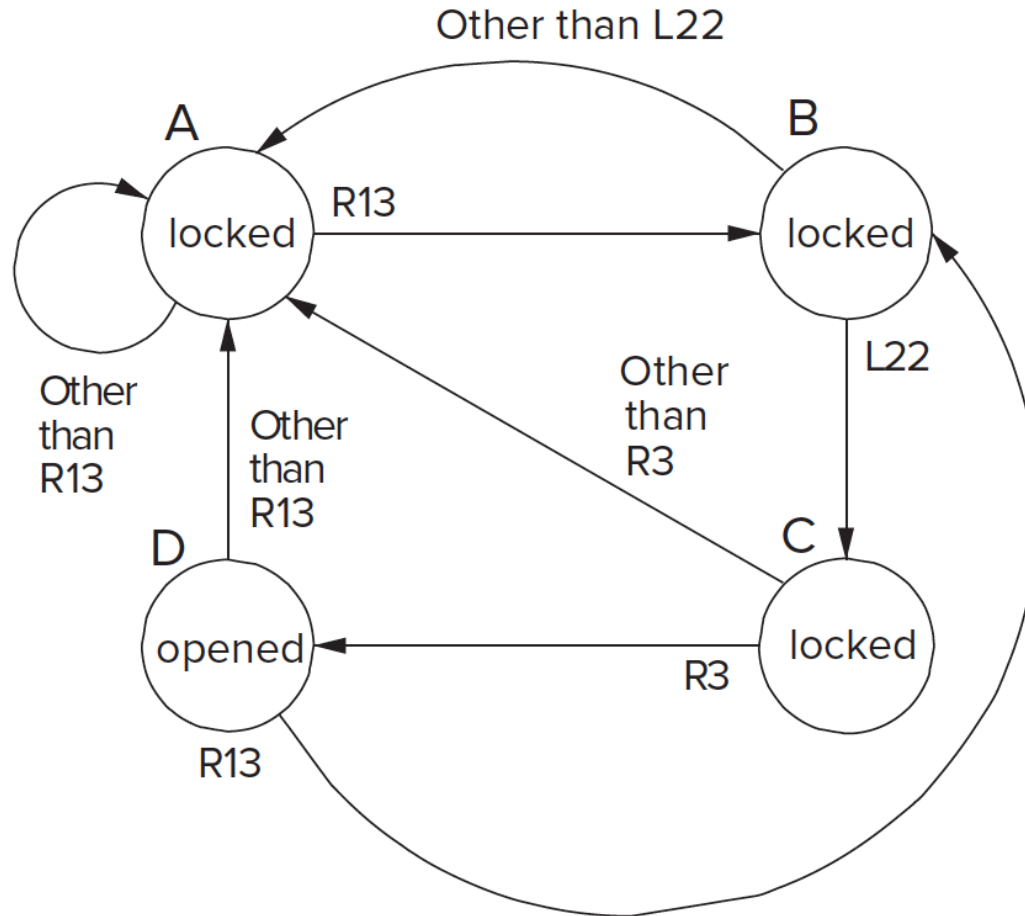- Completely describes the operation of the sequential lock




- We will understand "state diagrams" fully later today


Another Simple Example of State

- A standard Swiss traffic light has **4 states**

 - A. Green
- B. Yellow
- C. Red
- D. Red and Yellow



 - The sequence of these states are always as follows



Finite State Machines


- What is a **Finite State Machine** (FSM)?
 - **A discrete-time model** of a stateful system
 - Each state represents a snapshot of the system at a given time
- An FSM pictorially shows
 1. the set of all possible **states** that a system can be in
 2. how the system transitions from one state to another
- An FSM can model
 - A traffic light, an elevator, fan speed, a microprocessor, etc.
- **An FSM enables us to pictorially think of a stateful system using simple diagrams**

Finite State Machines (FSMs) Consist of:

■ Five elements:

1. A **finite** number of states
 - *State*: snapshot of all relevant elements of the system at the time of the snapshot
2. A **finite** number of external inputs
3. A **finite** number of external outputs
4. An explicit specification of all state transitions
 - How to get from one state to another
5. An explicit specification of what determines each external output value


State Transition Diagrams

 


★ = no buttons pressed

A state transition diagram is an abstract “graph” representation of a “state transition table”, where each state is represented as a node and each transition is represented as an arc.

 It represents the machine's behavior not its implementation!



Another Example : CPU controller

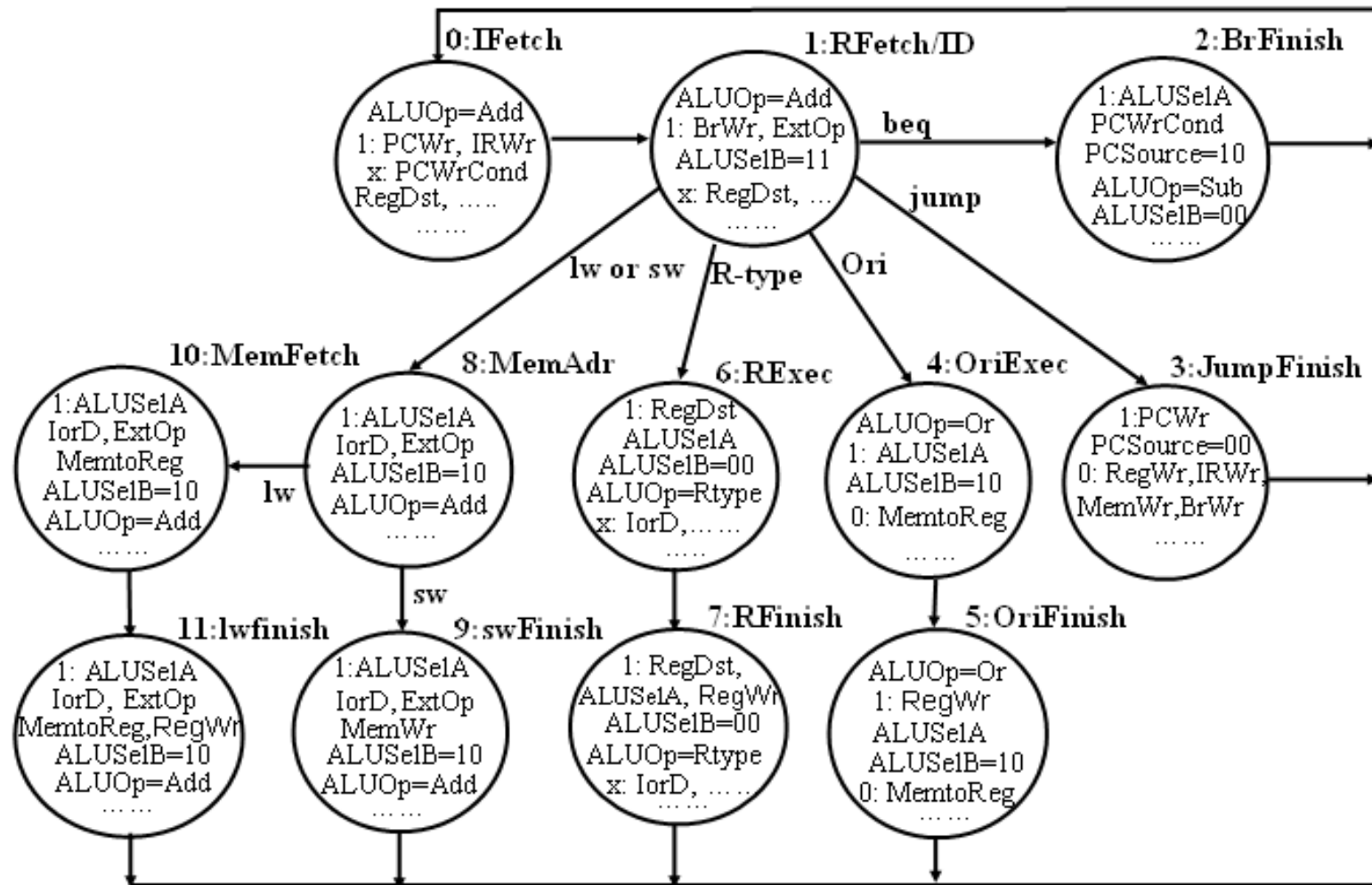

Constructing State Machines in Verilog

- We need register to hold
 - the current state
 - always @(posedge clk) block
 - We need next state function
 - Where do we go from each state given the inputs
 - state by state case analysis
 - next state determined by current state and inputs
 - We need the output function
 - State by state analysis
 - Moore: output determined by current state only
 - Mealy: output determined by current state and inputs
-

State Register


- Declare two values
 - state : current state – output of state register
 - nxtState : next state – input to state register
 - We rely on next state function to give us nxtState
- Declare symbols for states with state assignment

```
localparam IDLE=0, WAITFORB=1,  
           DONE=2, ERROR=3;
```

```
reg [1:0] state,    // Current state  
        nxtState; // Next state
```

State Register

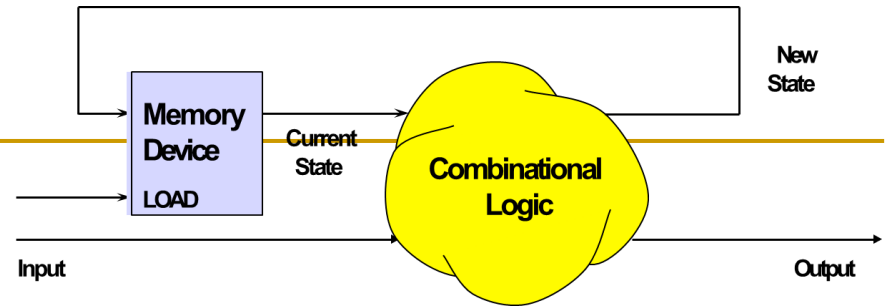- Simple code for register
- Define reset state
- Otherwise, just move to nxtState on clock edge



```
localparam IDLE=0, WAITFORB=1,
            DONE=2, ERROR=3;
reg [1:0] state,    // Current state
        nxtState; // Next state

always @(posedge clk) begin
    if (reset) begin
        state <= IDLE;    // Initial state
    end else begin
        state <= nxtState;
    end
end
```


Next State Function

- Combinational logic function
 - Inputs : state, inputs
 - Output : nxtState
 - We could use assign statements
 - We will use an always @(*) block instead
 - Allows us to use more complex statements
 - if
 - case
-

Next State Function

- Describe what happens in each state
- Case statement is natural for this

 
```
always @(*) begin
  nxtState = state; // Default next state: don't move
  case (state)
    IDLE : begin
      if (B) nxtState = ERROR;
      else if (A) nxtState = WAITFORB;
    end
    WAITFORB : begin
      if (B) nxtState = DONE;
    end
    DONE : begin
    end
    ERROR : begin
    end
  endcase
end
```



Output Function

- Describe the output of each state

 
```
always @(*) begin
  nxtState = state; // Default next state: stay where we are
  out = 0;          // Default output
  case (state)
    IDLE : begin
      if (B) nxtState = ERROR;
      else if (A) nxtState = WAITFORB;
    end
    WAITFORB : begin
      if (B) nxtState = DONE;
    end
    DONE : begin
      out = 1;
    end
    ERROR : begin
    end
  endcase
end
```



Edge Detector (Moore)


- Describe the output of each state
 
```
localparam A=0, B=1, C=2, D=4, E=5;  
reg [2:0] state,    // Current state  
        nxtState; // Next state  
  
always @(posedge clk) begin  
    if (reset) begin  
        state <= A;    // Initial state  
    end else begin  
        state <= nxtState;  
    end  
end
```



Edge Detector (Moore)

```
always @(*) begin
  nxtState = state;
  out = 0;
  case (state)
    A : if (in) nxtState = C;
        else    nxtState = B;
    B : if (in) nxtState = D;
    C : if (~in) nxtState = E;
    D : begin
        out = 1;
        if (in) nxtState = C;
        else    nxtState = E;
      end
    E : begin
        out = 1;
        if (in) nxtState = D;
        else    nxtState = B;
      end
    default : begin
        out = 1'bX;
        nxtState = 3'bX;
      end
  endcase
end
```

 

Summary

- **Please use “standard” FSM Verilog style shown here**
 - Do not be beguiled into thinking this is programming C!
 - **always @(posedge clk) block**
 - Use only for registers with simple logic
 - e.g. shifter, counter, enabled register, etc.
 - **Miscellaneous combinational logic**
 - assign statements (always safe)
 - always @(*) block (be very careful)
 - Think of this as a complex assign statement
 - Fine to have more than one
-